



**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**

## **FM RECEIVER**

**by**

**SANKALP JAIN**

**Roll no: 1813084**

**VIRAJ JAYDHE**

**Roll no : 1813085**

**DHAIRYA KATARIA**


**Roll no :1813091**

**Guide**

**MRS SWATI MAHAJAN**

**&**

**MR. Maruti Zalte**

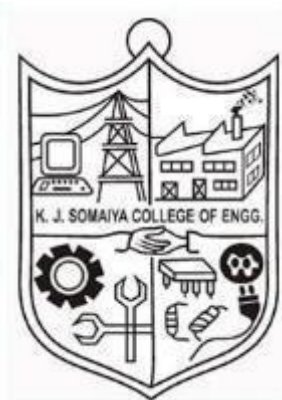

**DEPARTMENT OF ELECTRONICS &  
TELECOMMUNICATION**  
**K.J. SOMAIYA COLLEGE OF ENGINEERING,  
VIDYAVIHAR, MUMBAI-400077.**

**Department of Electronics and Telecommunication Engineering**



**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**

**Acknowledgement**

We would like to thank K.J. Somaiya College of Engineering for giving us this in-house internship. We express our gratitude towards Prof. Sandeep Sainkar for giving us this opportunity and his valuable guidance. We would like to thank Prof. Swati Mahajan and Prof. Maruti Zalte for allowing us to perform internships under Electronics and Telecommunication Engineering and helping us to select the related topics and projects. We would also thank EXTC HOD Dr. Amey Naik and Principal Dr. Shubha Pandit for creating such opportunities. Each of us have studied the concept through various information sources and tried our best to make this internship successful.

**Students involved:**

- ❖ Sankalp Jain (SY / B) 1813084
- ❖ Viraj Jedhe (SY / B) 1813085
- ❖ Dhairya Kataria (SY / B) 1813091



**K. J. Somaiya College of Engineering, Mumbai-77**  
(Autonomous College Affiliated to University of Mumbai)

<b>Index</b>	
<b>1. AIM.....</b>	<b>1</b>
<b>2. ABSTRACT.....</b>	<b>2</b>
<b>3. INTRODUCTION.....</b>	<b>3</b>
<b>4. FM RECEIVER.....</b>	<b>4</b>
<b>5. LITERATURE SURVEY.....</b>	<b>6</b>
<b>5.1. BRIEF DESCRIPTION OF DIFFERENT PARTS.....</b>	<b>6</b>
<b>5.2. LIST OF COMPONENTS.....</b>	<b>10</b>
<b>6. PROJECT DESIGN.....</b>	<b>11</b>
<b>6.1 .FM RECEIVER CIRCUIT EXPLANATION.....</b>	<b>11</b>
<b>6.2. RECEIVER CIRCUIT SNIPPETS.....</b>	<b>13</b>
<b>6.3. FREQUENCY MODULATION.....</b>	<b>15</b>
<b>6.4. WORKING OF CIRCUIT.....</b>	<b>16</b>
<b>7. CONCLUSION.....</b>	<b>17</b>
<b>8. REFERENCES.....</b>	<b>18</b>



**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**

**1.Aim**

- To learn more about Telecommunication Field.
- To use different software's.
- To learn and fabricate PCB.
- To develop team work.
- To test and debug electronic circuits.
- To learn more about devices involved in the communication field.
- To gain knowledge by doing projects.



**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**

**2.ABSTRACT**

Frequency modulation is the encoding of information in a carrier wave by varying the instantaneous frequency of the wave. The term and technology are used in computing, signal processing and telecommunications.

One should learn about FM modulation as it has many advantages like in FM receivers the noise can be reduced by increasing the frequency deviation and hence FM reception is immune to noise. FM transmitters are highly efficient. FM transmission can be used for the stereo sound transmission due to a large number of sidebands.

The project aims to enhance the learning of students. The circuit shows the working of FM receiver circuits. The project was built so that students can see the working of FM receiver and transmitter circuits without wasting time to build it on a breadboard. The project aims to reduce the hardships faced by students who do not know how to build circuits and for students who are not in the electronics field. The project aims to build a readymade FM receiver circuit for students.

The project takes into consideration all the required components and merges them to create a circuit board which can be used directly by students to enhance their learning.



**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**

### **3.INTRODUCTION**

This project was started with a goal to make a FM transmitter which was to be used with a FM receiver in our auditorium which receives signal from a mic, which would have made it easy for testing. Its carrier frequency range is from 460-970 MHZ. To work well with the receiver, the transmitter had to be of frequency in the middle of that range which is about 715 MHZ. Circuit diagrams for this transmitter was made, all components were available in the market, except for the oscillator for such high frequency, combined with the fact that receiver for such a high frequency is more susceptible to external noise when components would have been connected with wires and through hole components. While looking for lower frequency FM transmission in range 250-400 MHZ it was found that this range is used by police and other security in India, and creating such a transmitter would have interrupted with their signal and hence would have been safe.

The project was scaled down to making a FM receiver tuned to the frequency of a local FM music radio station. A circuit was designed, PCB was fabricated in the lab, while testing the results were not very clear due to connecting wires and other components picking up noise, which could have been improved further with the use of surface mounted components. We also created a FM modulation circuit which will make it easy for students to learn how FM modulation works without assembling the whole circuit themselves on a breadboard. This PCB is submitted in the Communication lab which will help as teaching aid for Frequency modulation.



**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**

#### **4. FM RECEIVER**

A radio or FM receiver is an electronic device that receives radio waves and converts the information carried by them to a usable form. An antenna is used to catch the desired frequency waves. The receiver uses electronic filters to separate the desired radio frequency signal from all the other signals picked up by the antenna, an electronic amplifier to increase the power of the signal for further processing, and finally recovers the desired information through demodulation. Of the radio waves, FM is the most popular one. Frequency modulation is widely used for FM radio broadcasting. It is also used in telemetry, radar, seismic prospecting, and monitoring newborns for seizures via EEG, two-way radio systems, music synthesis, magnetic tape-recording systems and some video-transmission systems. An advantage of frequency modulation is that it has a larger signal-to-noise ratio and therefore rejects radio frequency interference better than an equal power amplitude modulation (AM) signal.



**K. J. Somaiya College of Engineering, Mumbai-77  
(Autonomous College Affiliated to University of Mumbai)**

## **5.Literature Survey**

### **5.1.Brief description of different parts :-**


#### **1. IC LM-386:-**



*Figure 1 IC LM386*

The IC LM386 is a low-power audio amplifier, and it utilizes low **power supply** like batteries in electrical and **electronic circuits**. This IC is available in the package of mini 8-pin DIP. The voltage gain of this amplifier can be adjusted to 20, and the voltage gain will be enhanced to 200 by employing external components like resistors as well as capacitors among the pins 1 & 8.

#### **2. BJT BF494,495:-**

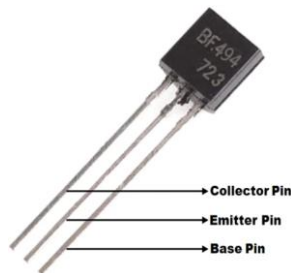

*Figure 2 BJT BF494*

General purpose radio frequency transistors BF 494,495 are used for obtaining FM modulation.





**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**

### **3.Capacitors:-**



*Figure 3 Capacitor*

A capacitor is a device that stores electrical energy in an electric field. It is a passive electronic component with two terminals. The effect of a capacitor is known as capacitance.

### **4.Resistors:-**



*Figure 4 Resistor*

A resistor is a passive two-terminal electrical component that implements electrical resistance as a circuit element. In electronic circuits, resistors are used to reduce current flow, adjust signal levels, to divide voltages, bias active elements, and terminate transmission lines, among other uses.

### **5.Variable Resistance:-**

**Department of Electronics and Telecommunication Engineering**



**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**



*Figure 5 Variable Resistance*

A resistor of which the ohmic resistance value can be adjusted. Either mechanically (**potentiometer**, **rheostat**) or electronically (**digital potentiometer**).

## **6. Variable Capacitor:-**



*Figure 6 Variable Capacitance*

A variable capacitor is a **capacitor** whose capacitance may be intentionally and repeatedly changed mechanically or electronically. Variable capacitors are often used in **L/C circuits** to set the resonance frequency, e.g. to tune a radio (therefore it is sometimes called a tuning capacitor or tuning condenser), or as a variable reactance, e.g. for **impedance matching** in **antenna tuners**.



**K. J. Somaiya College of Engineering, Mumbai-77  
(Autonomous College Affiliated to University of Mumbai)**

**7. Speaker:-**



*Figure 7 Speaker*

Speakers are transducers that convert electromagnetic waves into sound waves. The speakers receive audio [input](#) from a device such as a computer or an audio receiver. This input may be either in [analog](#) or [digital](#) form. Analog speakers simply amplify the analog electromagnetic waves into sound waves. Since sound waves are produced in analog form, digital speakers must first convert the digital input to an analog signal, then generate the sound waves.



**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**

### **5.2.List of Components**

- IC- LM386
- T1 BF494
- T2 BF495
- 4 turn 22SWG 4mm dia air core
- C1 220nF
- C2 2.2nF
- C 100nF \* 2
- C4 10uF
- C5 10uF (25 V)
- C7 47nF
- C8 220 uF(25 V)
- C9 100 uF (25 V) \* 2
- R 10K $\Omega$  \* 2
- R3 1K $\Omega$
- R4 10 $\Omega$
- Variable resistance
- Variable capacitance
- Speaker
- Switch
- Antenna
- Battery

**Department of Electronics and Telecommunication Engineering**






**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**

full FM bandwidth (88-108 MHz), try changing the value of VC. Its capacitance is to be determined experimentally.

The self-supporting coil L has four turns of 22 SWG enameled copper wire, with air core having a 4mm internal diameter. It can be constructed on any cylindrical object, such as a pencil or pen, having a diameter of 4 mm. When the required number of turns of the coil has reached, the coil is taken off the cylinder and stretched a little so that the turns don't touch each other.

Capacitors C3 (100nF) and C10 (100 $\mu$ F, 25V), together with R3 (1k), comprise a band-pass filter for very low frequencies, which is used to separate the low-frequency signal from the high-frequency signal in the receiver.

## **6.2 RECEIVER CIRCUIT SNIPPETS**

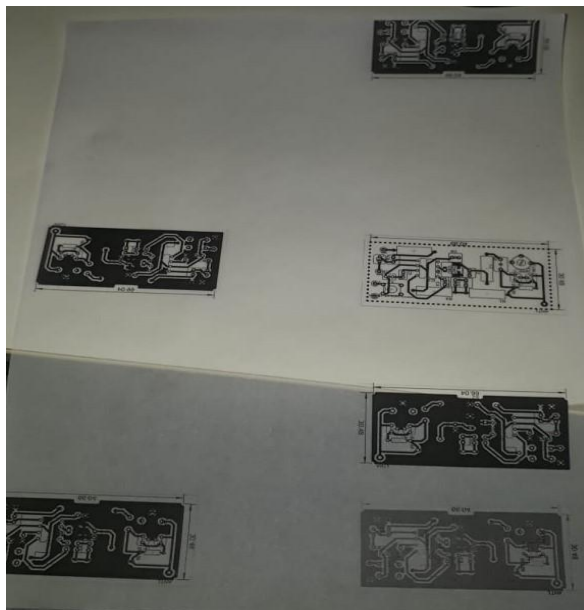


*Figure 9 PCB Layout of FM Receiver*



**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**



*Figure 10 Front Side of PCB*

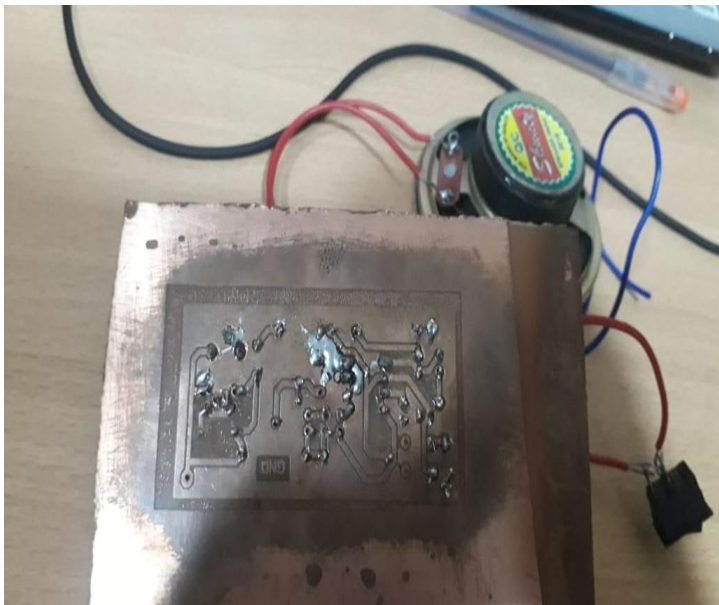

*Figure 11 Tracks (Backside of PCB)*

**Department of Electronics and Telecommunication Engineering**


### **6.3.FM Modulation**

The above circuit was not able to receive the FM signals. We were unable to identify the problem as the circuit was a bit tricky and complex to build. So instead we decided to build the sub part of FM Receiver i.e. Frequency modulation using IC 8038.

The process, in which the frequency of the carrier is varied in accordance with the instantaneous amplitude of the modulating signal, is called 'Frequency Modulation'. The FM signal is expressed as:

$$S(t) = A_c \cos(2\pi f_c t + \beta \sin(2\pi f_m t))$$

Where  $A_c$  is amplitude the carrier signal,  $f_c$  is the carrier frequency  $f_m$  is the modulation index of the FM wave.

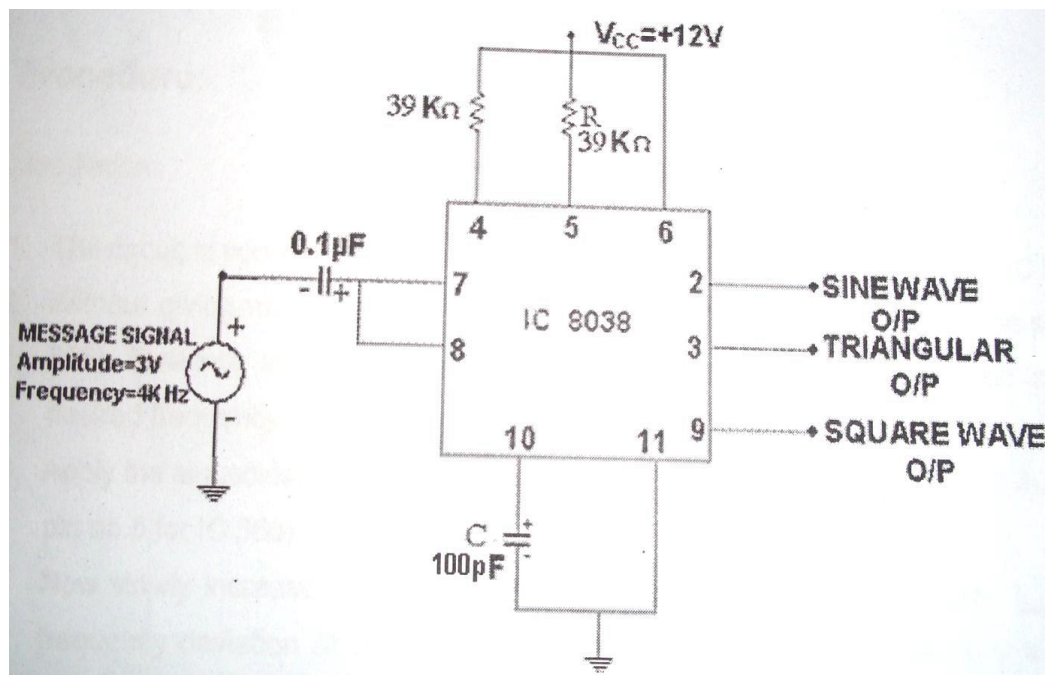

*Figure 12 Frequency Modulator*






**K. J. Somaiya College of Engineering, Mumbai-77**  
(Autonomous College Affiliated to University of Mumbai)

#### **6.4. Working of circuit**

1. The circuit is connected as per the circuit diagram shown in Fig.2
2. Without giving modulating signals observe the carrier signal at pin no.2 . Measure amplitude and frequency of the carrier signal. To obtain a carrier signal of desired frequency, find the value of R from  $f=1/(2\pi RC)$  taking  $C=100\text{pF}$ .
3. Apply the sinusoidal modulating signal of frequency 4 KHz and amplitude 3Vp-p at pin no. 7. (pin no. 5 for IC566)
4. Now slowly increase the amplitude of modulating signal and measure  $f_{\min}$  and maximum frequency deviation  $\Delta f$  at each step. Evaluate the modulating index ( $m_f=\beta$ ) using  $\Delta f/f_m$  where  $\Delta f=|f_c-f_{\min}|$ . Calculate Band width.  $BW=2(\beta+1)f_m=2(\Delta f+f_m)$
5. Repeat step 4 by varying the frequency of the modulating signal.

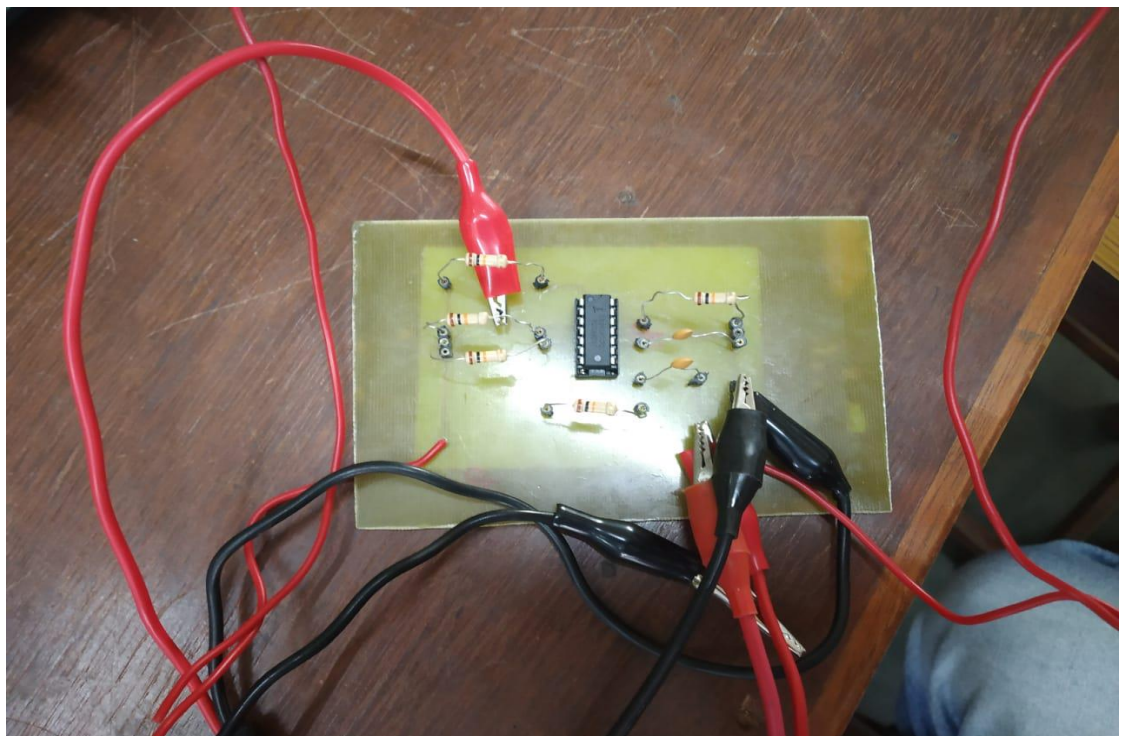


*Figure 13 Frequency Modulator Circuit*



**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**



*Figure 14 Setup of Testing*

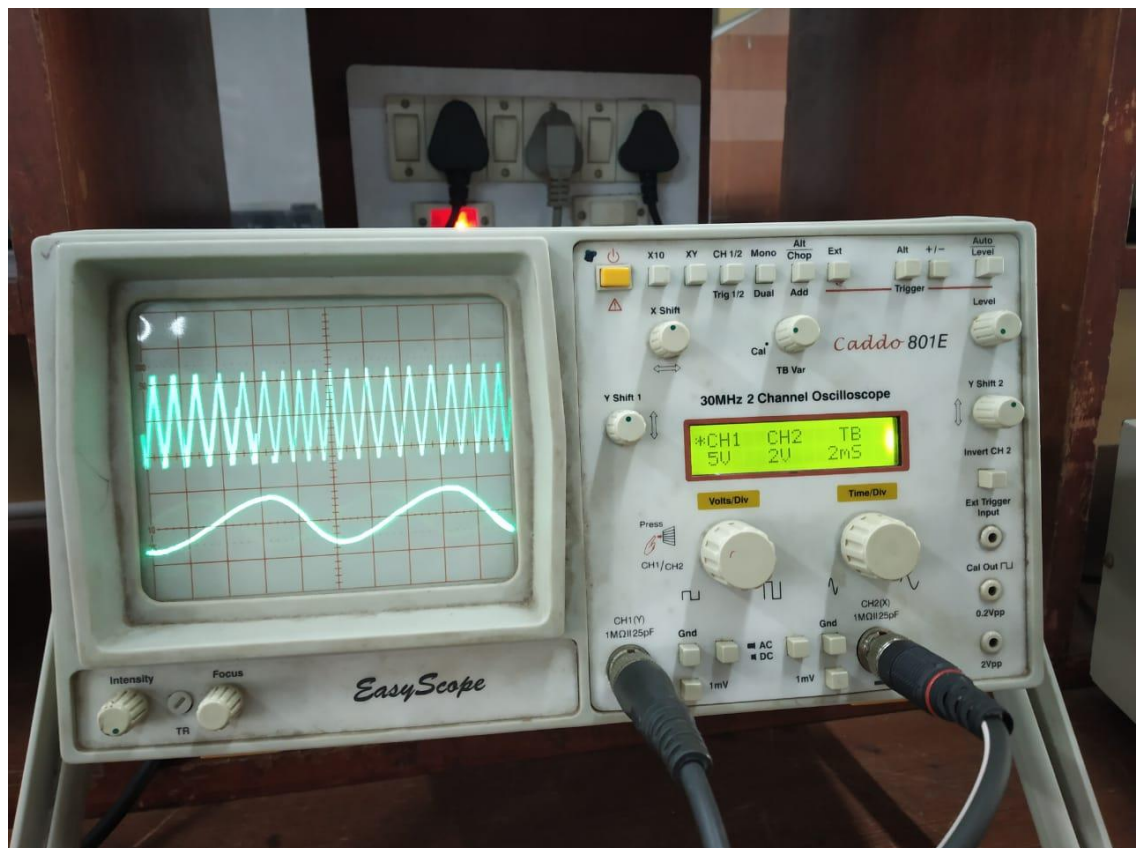

*Figure 15 Output*

**Department of Electronics and Telecommunication Engineering**



**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**

### **7. Conclusion**

From this project we learned to divide the project on smaller parts and work on it as a team. We learned the functioning of FM receivers. In this project we reviewed the whole pipeline, like how we must move to build a small functioning circuit board. The pipeline is as follows:-i. Understanding the concept, ii. Simulating the circuit, iii. Designing the circuit, iv. Testing the circuit. We learned the working of FM receivers along with its circuit and learned about various kinds of parts needed to build it. We learned how frequency-based circuits require more ground on board to avoid noise. We learned how SMD (surface mounted devices ) can be used instead of regular devices to avoid noise in frequency-based circuits. We learned the designing of circuits on LTSPICE. We learned how to simulate the circuit before building it. We learned the required procedure required for building a good circuit board. From this project we learned building PCB of circuits. We learned how to overcome the difficulties faced during PCB building. At last we learned a lot from this project.



**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**

### **8. References**

1. Rider & Usan; FM Transmission & Reception; J.F. Rider publication; 1950 second edition
2. Joseph J. Carr; Secrets of RF circuit design; McGraw-Hill Inc., US; 2nd edition edition (1 December 1996)
3. <https://electronicsforu.com/electronics-projects/simple-fm-receiver>
4. <https://www.electroschematics.com/small-fm-receiver/>
5. [https://en.wikipedia.org/wiki/Radio\\_receiver](https://en.wikipedia.org/wiki/Radio_receiver)
6. <https://www.instructables.com/id/How-to-Make-FM-Transmitter/>
7. <https://eeepproject.com/fm-transmitter-circuit/>